

Two ways to think about logic signals

- Fixed logic convention
 - High voltage always means 1, TRUE, Asserted
 - Low voltage always means 0, FALSE, Negated
- Mixed Logic convention
 - Can have High and Low true signals
 - High true signals means that high voltage means 1, True, asserted
 - Low true signals means that low voltage means 1, True, asserted
 - In **real world**, have both high and low true signals.

BR 1/99

1

High True vs. Low True Logic

- Different ways to say that a signal is **high** true
 - Is high if signal is TRUE, is low if signal is FALSE
 - Is high if signal is 1, is low if signal is 0
 - Is high if signal is *asserted*, is low if signal is *negated*
- Different ways to say that a signal is **low** true
 - Is low if signal is TRUE, is high if signal is FALSE
 - Is low if signal is 1, is high if signal is 0
 - Is low if signal is *asserted*, is high if signal is *negated*

BR 1/99

2

Asserted vs. Negated

- **Asserted** ALWAYS means that a signal is TRUE or logic 1.
 - Logic 1 could be represented by a HIGH voltage (high true)
 - Logic 0 could be represented by LOW voltage (low true)
- **Negated** ALWAYS means that a signal is FALSE or logic 0.
 - Logic 0 could be represented by a LOW voltage (high true)
 - Logic 1 could be represented by a HIGH voltage (low true)

BR 1/99

3

The Physical World



When a button is pressed, it is asserted (true). However, its physical construction may output this as a LOW VOLTAGE (low true!!!)

To the person pressing the button, they don't know and don't care that a low voltage is output when the button is pressed. They just know they have ASSERTED the button.

BR 1/99

4



THE Problem

Have two buttons, each button outputs a low voltage (L) when pressed.

Button A



Button B

  


Want a Voltage Gate that outputs a 'H' when both buttons are ASSERTED.

The rest of the lecture will be devoted to determining the answer.....

BR 1/99


5

Examples of high, low signals

 

Switch open (negated), output is L

High True button (switch)

 

Switch closed (asserted), output is H

BR 1/99

6

Examples of high, low signals

Switch open (negated),
output is H

Switch closed (asserted),
output is L

BR 1/99 7

7400 Logic Gate

A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

AND gate with high true inputs,
low true output

		High True	Low True
A	B	Y	
0	0	0	AND
0	1	0	
1	0	0	
1	1	1	

A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

OR gate with low true inputs,
high true output

		Low True	High True
A	B	Y	
1	1	1	OR
1	0	1	
0	1	1	
0	0	0	

BR 1/99 8

Fixed Logic Polarity vs Mixed Logic Polarity

- In Fixed logic polarity, every signal is considered high true.
- In Mixed logic polarity, can have high, low true signals.
 - Low true signal names followed by '(L)' to indicate low true

BR 1/99 9

Fixed Polarity vs Mixed Polarity


- NAND, AND
 - Fixed: $(AB)'$ is read as "A nand B"
 - Mixed: $(AB) (L)$ is read "A and B, low true".
- NOR, OR
 - Fixed: $(A+B)'$ is read as "A nor B"
 - Mixed: $(A+B) (L)$ is read "A or B, low true".
- NOT
 - Fixed: $(A)'$ is read as "NOT A"
 - Mixed: $(A) (L)$ is read as "A, low true "

BR 1/99


10

7404 Logic Gate

A	Y
L	H
H	L

 

 Buffer that converts high true input to low true output



Buffer that converts low true input to high true output

High True Low True

A	Y
0	0
1	1

Low True High True


A	Y
1	1
0	0

BR 1/99


11

7402 Logic Gate

A B	Y
L L	H
L H	L
H L	L
H H	L

 

 OR gate with high true inputs, low true output



AND gate with low true inputs, high true output

High True Low True

A B	Y
0 0	0
0 1	1
1 0	1
1 1	1

OR

Low True High True

A B	Y
1 1	1
1 0	0
0 1	0
0 0	0


AND

BR 1/99

12

7408 Logic Gate

A	B	Y
L	L	L
L	H	L
H	L	L
H	H	H

 


AND gate with high true inputs,
high true output

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

High True High True
AND

A(L)	B(L)	(A + B) (L)
1	1	1
1	0	1
0	1	1
0	0	0

Low True Low True
OR

 


OR gate with low true inputs,
low true output

BR 1/99 13

7432 Logic Gate

A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H

 


OR gate with high true inputs,
high true output

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

High True High True

A(L)	B(L)	(AB)(L)
1	1	1
1	0	0
0	1	0
0	0	0


Low True Low True

 

AND gate with low true inputs,
low true output

BR 1/99 14


Problem #1

 

Two low true switches. When either switch A or switch B is asserted (pressed), want Y to be asserted. Y is high true.

BR 1/99 15


Problem #1 (solution)

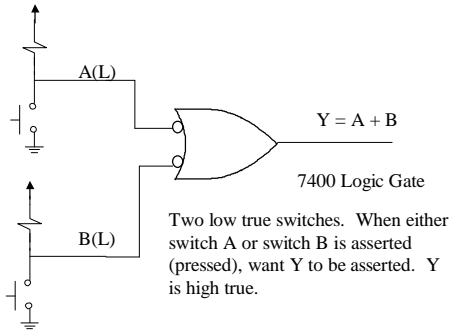

BR 1/99

16


Problem #2

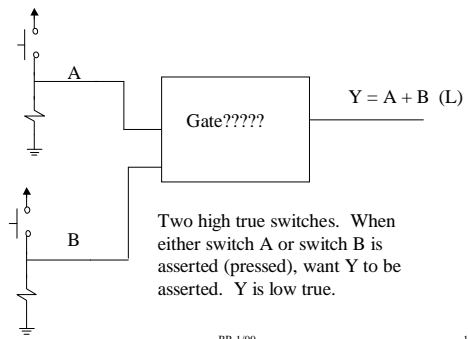

BR 1/99

17

Problem #2 (solution)

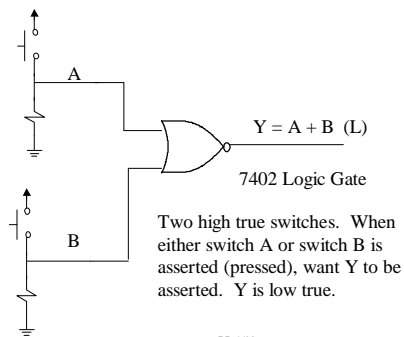

BR 1/99

18

Problem #3

Two low true switches. When both switch A and switch B is asserted (pressed), want Y to be asserted. Y is low true.

BR 1/99 19

Problem #3 (solution)

Two low true switches. When both switch A and switch B is asserted (pressed), want Y to be asserted. Y is low true.

7432 Logic Gate

BR 1/99 20

THE Problem (again)

Have two buttons, each button outputs a low voltage (L) when pressed.

Button A

Button B

Want a Voltage Gate that outputs a 'H' when both buttons are ASSERTED.

Solution?????

BR 1/99 21

THE Problem (solution)

Have two buttons, each button outputs a low voltage (L) when pressed.

Button A

Button B

7402 Gate

Want a Voltage Gate that outputs a 'H' when both buttons are ASSERTED.

When both A and B asserted (low true), output is asserted (high true)

BR 1/99 22

Mixed High True, Low True Inputs

A(L)

B

Gate????

Y = AB (L)

One low true switch and one high true switch. When both switch A and switch B is asserted (pressed), want Y to be asserted. Y is low true.

BR 1/99 23

Mixed High True, Low True Inputs

A(L)

B

Y = AB (L)

Hmmm... What is this? This does not match any of our gate types. We will have to convert one the gate inputs so that either we have BOTH high true inputs or BOTH low true inputs.

BR 1/99 24

Mixed High True, Low True Inputs

Solution #1: Convert both gate inputs to low true.

Now we have a two input gate with both inputs low true. We can now match this to one of our two input gates.

BR 1/99 25

Mixed High True, Low True Inputs

Solution #2: Convert both gate inputs to high true.

Now we have a two input gate with both inputs high true. We can now match this to one of our two input gates.

BR 1/99 26

<table border="1"> <tr><th>A</th><th>B</th><th>Y</th></tr> <tr><td>L</td><td>L</td><td>L</td></tr> <tr><td>L</td><td>H</td><td>L</td></tr> <tr><td>H</td><td>L</td><td>L</td></tr> <tr><td>H</td><td>H</td><td>L</td></tr> </table>	A	B	Y	L	L	L	L	H	L	H	L	L	H	H	L	7408		
A	B	Y																
L	L	L																
L	H	L																
H	L	L																
H	H	L																
<table border="1"> <tr><th>A</th><th>B</th><th>Y</th></tr> <tr><td>L</td><td>L</td><td>L</td></tr> <tr><td>L</td><td>H</td><td>H</td></tr> <tr><td>H</td><td>L</td><td>H</td></tr> <tr><td>H</td><td>H</td><td>H</td></tr> </table>	A	B	Y	L	L	L	L	H	H	H	L	H	H	H	H	7432		
A	B	Y																
L	L	L																
L	H	H																
H	L	H																
H	H	H																
<table border="1"> <tr><th>A</th><th>B</th><th>Y</th></tr> <tr><td>L</td><td>L</td><td>H</td></tr> <tr><td>L</td><td>H</td><td>H</td></tr> <tr><td>H</td><td>L</td><td>H</td></tr> <tr><td>H</td><td>H</td><td>L</td></tr> </table>	A	B	Y	L	L	H	L	H	H	H	L	H	H	H	L	7400		
A	B	Y																
L	L	H																
L	H	H																
H	L	H																
H	H	L																
<table border="1"> <tr><th>A</th><th>B</th><th>Y</th></tr> <tr><td>L</td><td>L</td><td>H</td></tr> <tr><td>L</td><td>H</td><td>L</td></tr> <tr><td>H</td><td>L</td><td>L</td></tr> <tr><td>H</td><td>H</td><td>L</td></tr> </table>	A	B	Y	L	L	H	L	H	L	H	L	L	H	H	L	7402		
A	B	Y																
L	L	H																
L	H	L																
H	L	L																
H	H	L																


Gate Summaries

BR 1/99 27

Complete Logic Families

- A set of logic gates is *complete* if it can implement any boolean function.
 - Must be able to implement AND, OR, NOT function to be complete

 The 7400 gate is complete all by itself!!!!




BR 1/99

28

Other Complete Logic Families

 The 7402 gate is also complete all by itself.




Any boolean equation can be implemented using either just 7400 gates or just 7402 gates.

BR 1/99


29

Other Complete Logic Families (cont)

 The 7408 and 7404 together make a complete family.



 The 7432 and 7404 together make a complete family.



BR 1/99


30

Sum of Products


- A boolean equation in the form:
 $f = \text{and_term} + \text{and_term} \dots + \text{and_term}$
 is called a *Sum of Products* (SOP).

$$Y = AB + CD$$

 Implementing this logic in two levels of gating is easy.



And-Or form

 

Nand-Nand form drawn in mixed logic convention

BR 1/99


31

Product of Sums


- A boolean equation in the form:
 $f = (\text{or_term})(\text{or_term})\dots(\text{or_term})$
 is called a *Product of Sums* (POS).

$$Y = (A+B)(C+D)$$

 Implementing this logic in two levels of gating is easy.



Or-And form

 

Nor-Nor form drawn in mixed logic convention

BR 1/99

32

What do you have to know?

- Definitions of Assertion, Negation, High-True, Low-true
- Low, High true switch construction
- Low, High True boolean functions of Voltage gates
- Problems in the form of the switch problems given in these notes
- Complete Logic Families
- NAND-NAND form drawn in mixed logic. NOR-NOR form drawn in mixed logic.

BR 1/99

33
